




# **Embedded Systems** **(EPM)**

---

**Lecture (10) Summary**

# PID-Controller

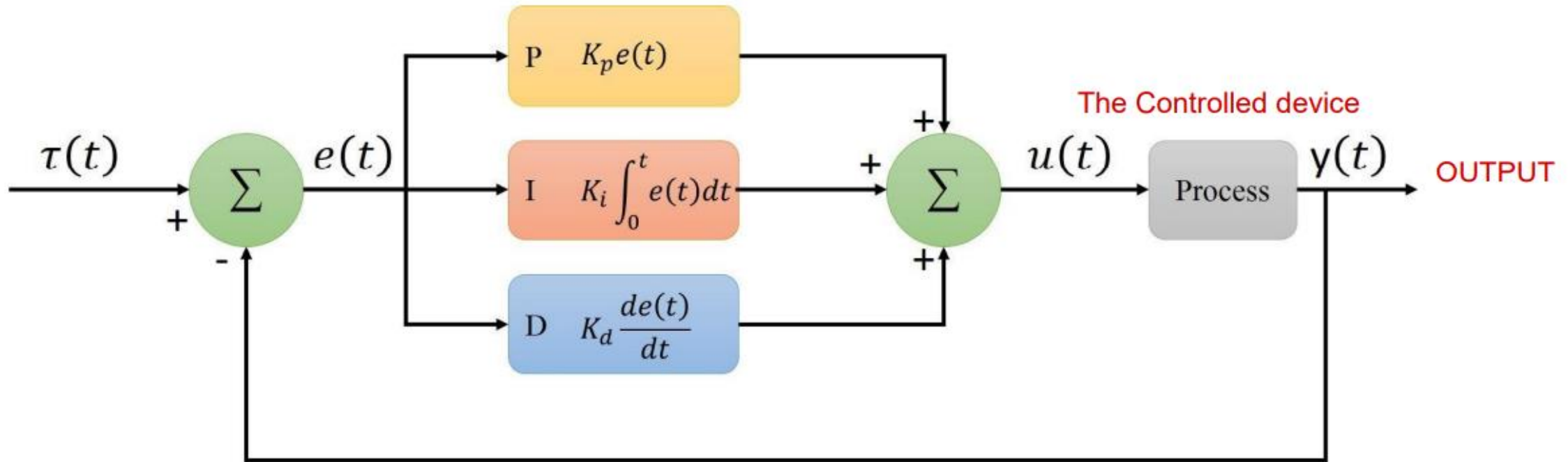

$$u(t) = K_p e(t) + K_i \int_0^t e(t) dt + K_d \frac{de(t)}{dt}$$

## 1- Proportional term:

$$K_p e(t)$$


produces an output value that is proportional to the current error value. The proportional response can be adjusted by multiplying the error by a constant  $K_p$ , called the proportional gain constant.

A high proportional gain results in a large change in the output for a given change in the error. If the proportional gain is too high, the system can become unstable.

a small gain results in a small output response to a large input error.

If the proportional gain is too low, the control action may be too small when responding to system disturbances
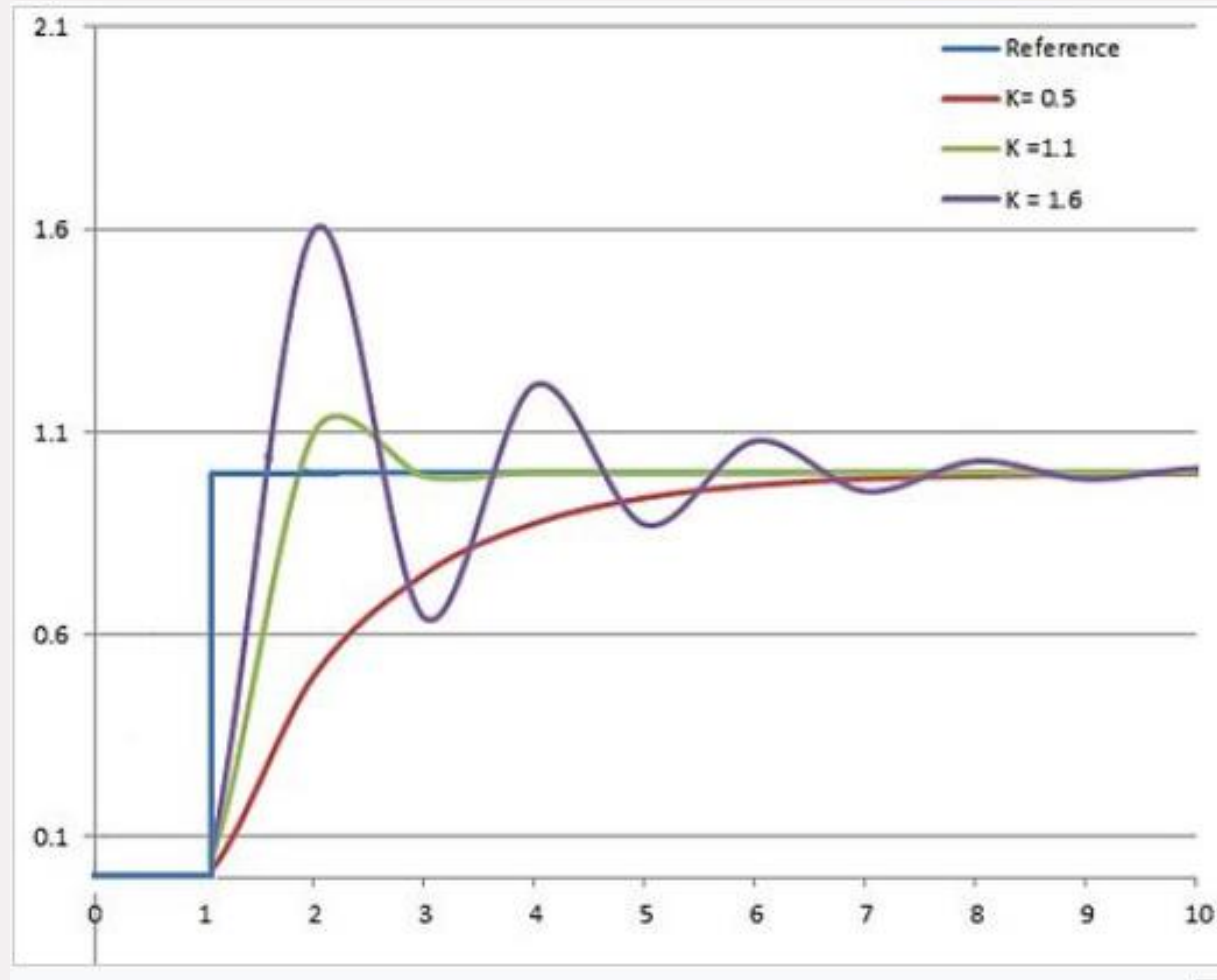
## By Changing the values of $K_p$ at const $K_i$ , $K_d$ :



## **2- Integral term:**

$$K_i \int_0^t e(t) dt$$

The integral in a PID controller is the sum of the instantaneous error over time and gives the accumulated offset that should have been corrected previously.


It's proportional to both the magnitude of the error and the duration of the error.

The accumulated error is then multiplied by the integral gain ( $K_i$ ) and added to the controller output.

It accelerates the movement of the process towards setpoint and eliminates the residual steady-state error that occurs with a pure proportional controller.

since the integral term responds to accumulated errors from the past, it can cause the present value to overshoot the setpoint value
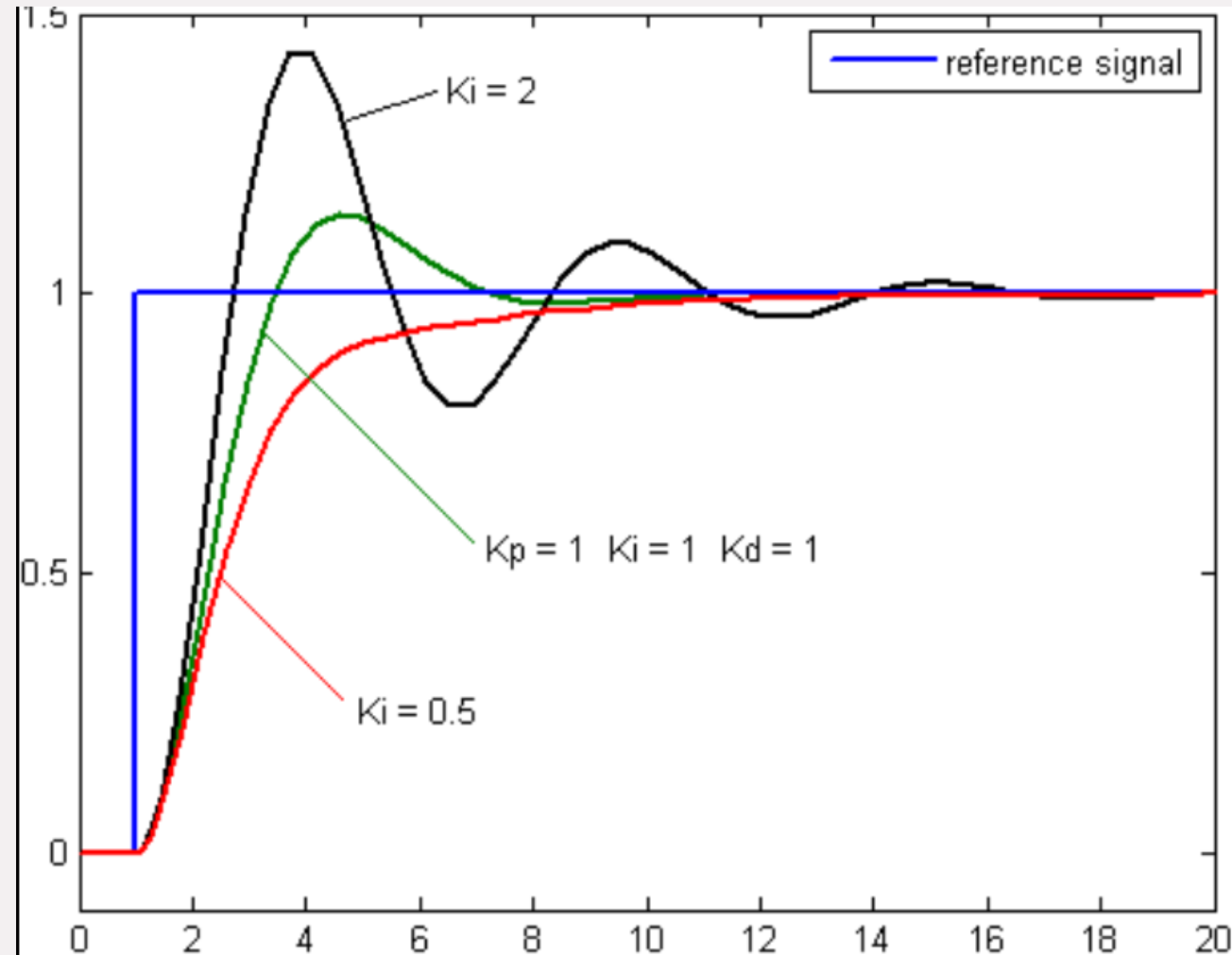
## By Changing the values of $K_i$ at const $K_p$ , $K_d$ :




### 3- Proportional term:

$$K_d \frac{de(t)}{dt}$$

it is calculated by determining the slope of the error over time and multiplying this rate of change by the derivative gain  $K_d$ .

It predicts system behavior and thus improves settling time and stability of the system.

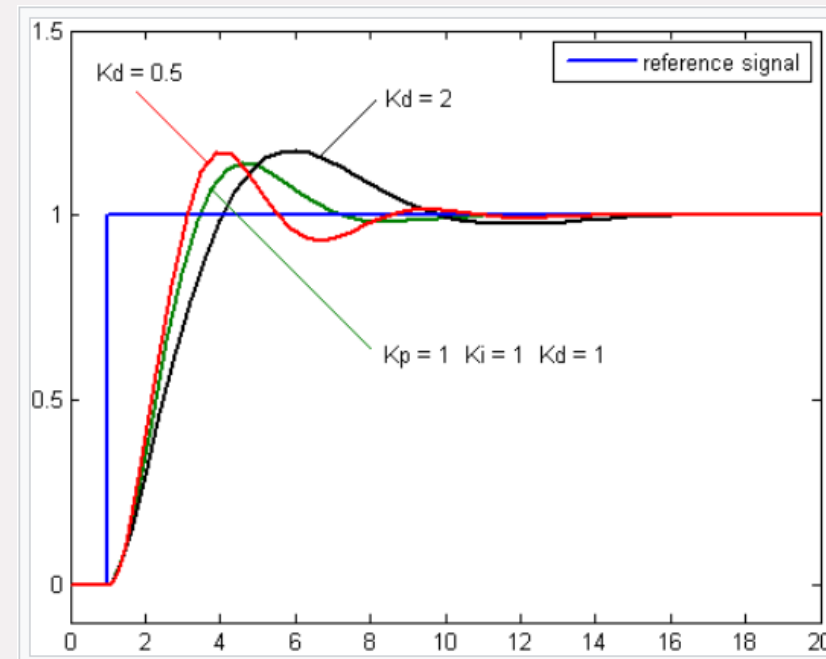By Changing the values of  $K_d$  at const  $K_p$ ,  $K_i$ :



# Realization of PID

```
213 float r=50;
214 float ui,up,ud;
215 float ui_old;
216 float e;
217 float e_old;
218 float u;
219 float Kp=5; float Ki=0; float Kd=0;
220 void loop(void) {
221     float h=read_val();
222     e=r-h;
223     up=Kp*e;
224     ui=ui+Ki*e;
225     ud=Kd*(e-e_old);
226     u=up+ui+ud;
227     e_old=e;
228     set_val(u);
229     delay(10);
230 }
```

Reading Output Value

Comparing it to the set point

Control based on proportional action

integral action

diffrential action

Total action on system


and repeat the loop



# Realization of PID With (Anti-windup)



```
213 float r=50;
214 float ui,up,ud;
215 float ui_old;
216 float e;
217 float e_old;
218 float u;
219 float Kp=30; float Ki=0.75; float Kd=20;
220 #define MAX_U 100
221 #define MIN_U 0
222 void loop(void) {
223     float h=read_val();
224     e=r-h;
225     up=Kp*e;
226     ui=ui+Ki*e;
227     ud=Kd*(e-e_old);
228     u=up+ui+ud;
229     if ( (u>MAX_U) || (MIN_U<0) ) {
230         ui=ui_old;
231         u=up+ui+ud;
232     }
233     e_old=e;
234     ui_old=ui;
235     set_val(u);
236     if (digitalRead(SET_POINT_PIN)==0) r=get_set_point();
237     delay(10);
238 }
```

$u < \text{MIN\_U}$

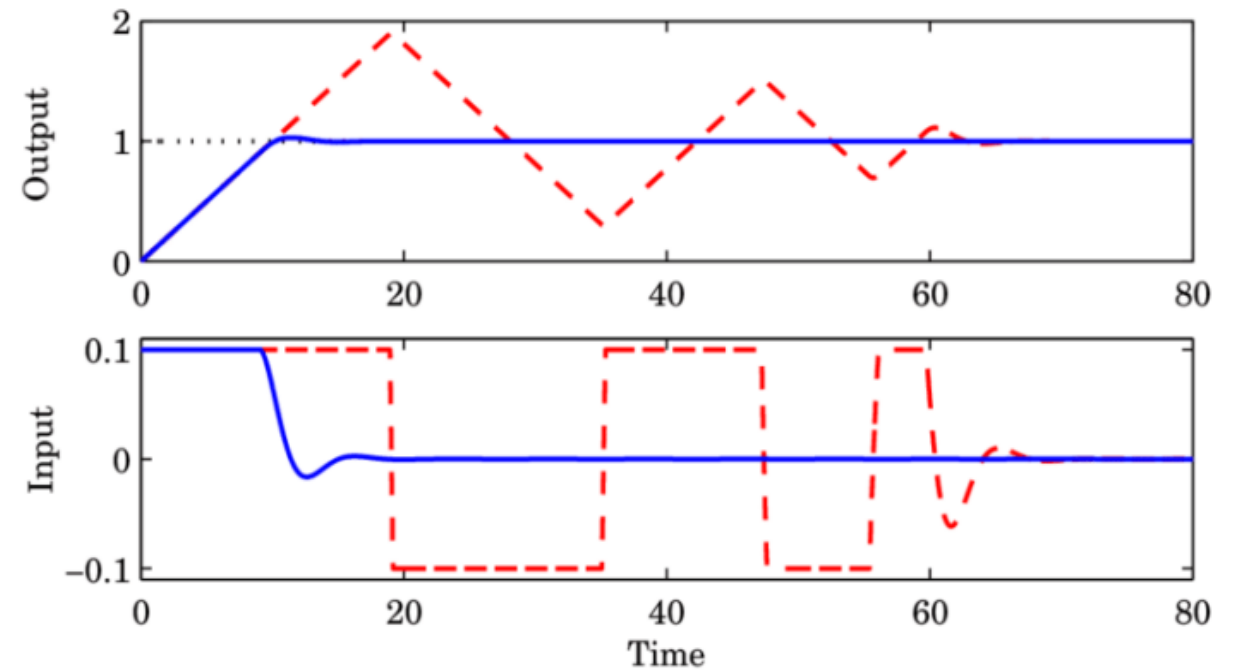

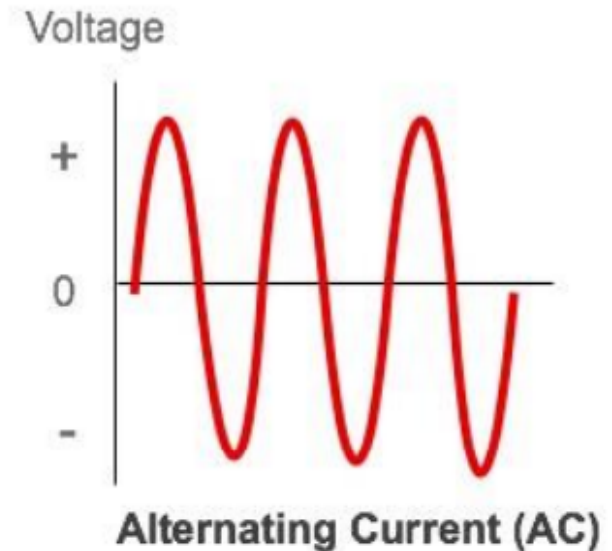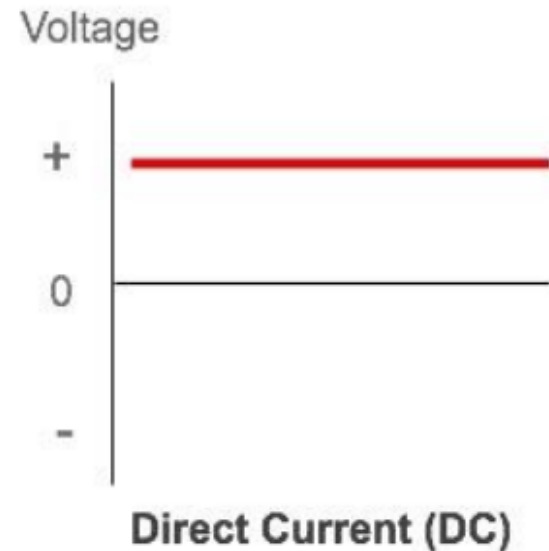
# Rectifier

- A rectifier is an electrical device that **converts** alternating current **(AC)**, which periodically reverses direction, to direct current **(DC)**, which flows in only one direction.


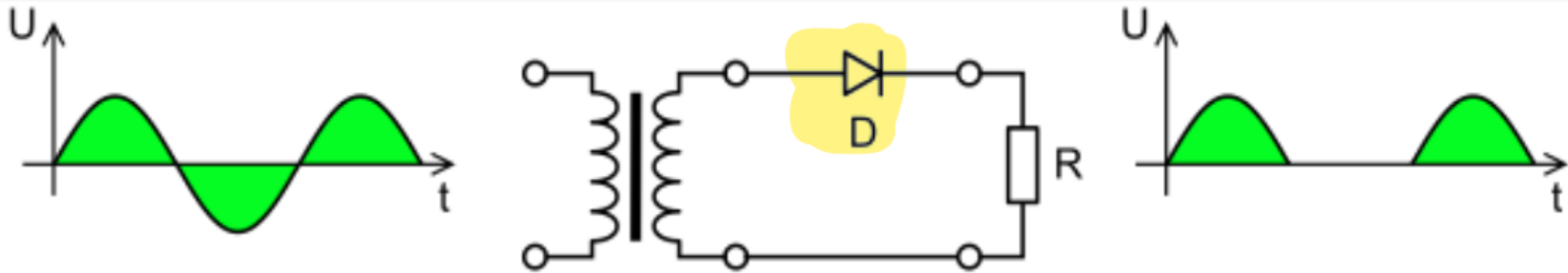
# Rectifier


Single-phase rectifiers (Half-wave rectification)



- In half-wave rectification of a single-phase supply, either the positive or negative half of the AC wave is passed, while the other half is blocked. Because only one half of the input waveform reaches the output, mean voltage is lower. Half-wave rectification requires a single diode in a single-phase supply

# Rectifier
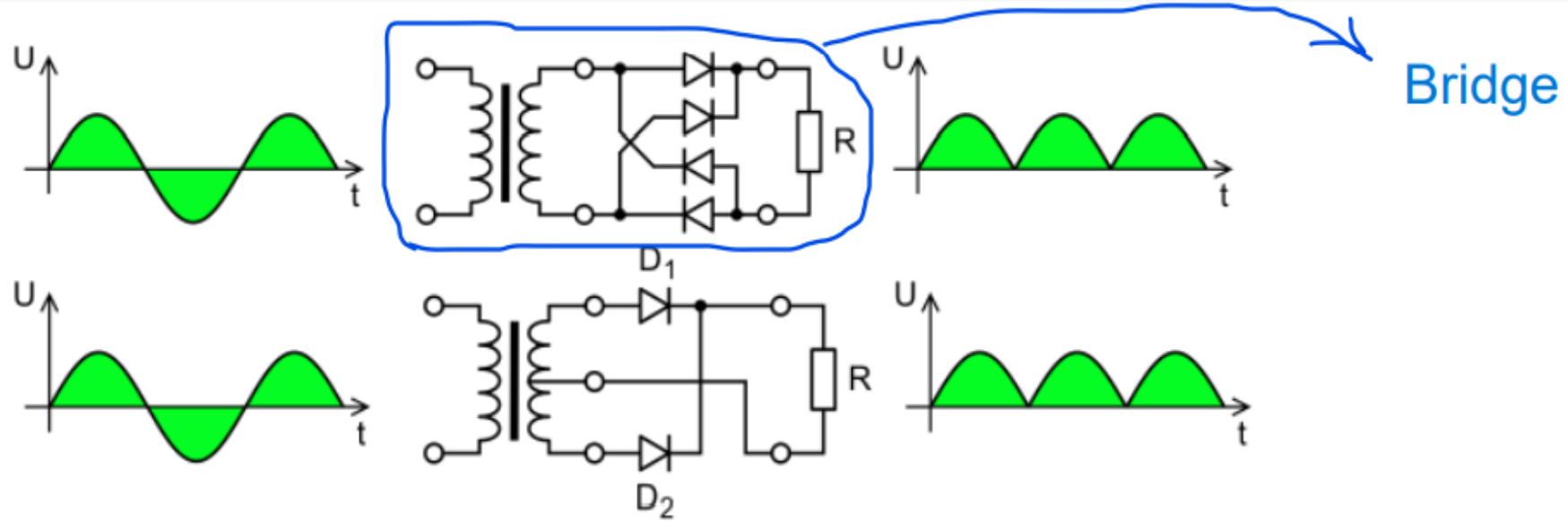
## Single-phase rectifiers (Full-wave rectification)






- A full-wave rectifier converts the whole of the input waveform to one of constant polarity (positive or negative) at its output. Mathematically, this corresponds to the absolute value function.
- Full-wave rectification converts both polarities of the input waveform to pulsating DC (direct current), and yields a higher average output voltage.

# Rectifier

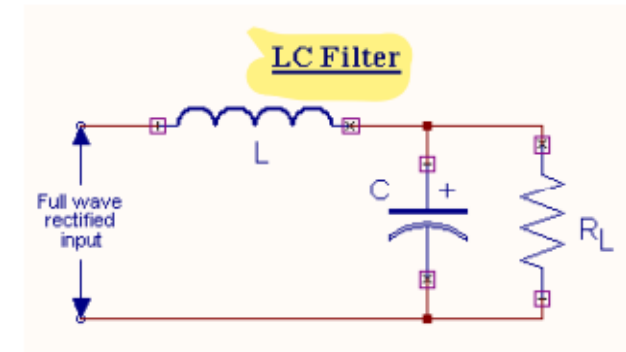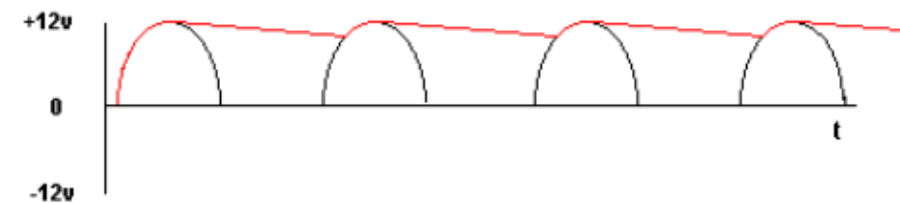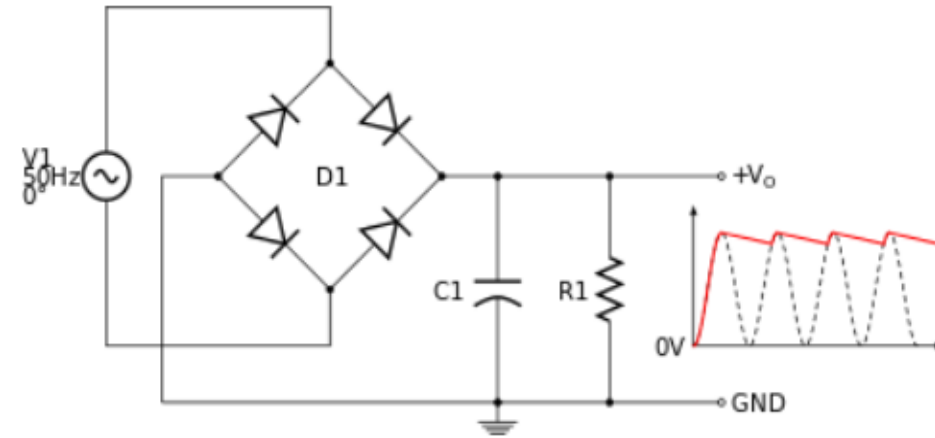
## Output smoothing (Filtering)

- While half-wave and full-wave rectification deliver **unidirectional current**, neither produces a constant voltage.
- There is a large **AC ripple** voltage component at the source frequency for a **half-wave rectifier**, and **twice** the source frequency for a **full-wave rectifier**.
- Ripple voltage is usually specified **peak-to-peak**.
- Producing steady DC from a rectified AC supply requires a **smoothing circuit** or **filter**. In its simplest form this can be just a **capacitor** (also called a **filter**, reservoir, or **smoothing capacitor**)







# Effect of small/large cutoff frequency

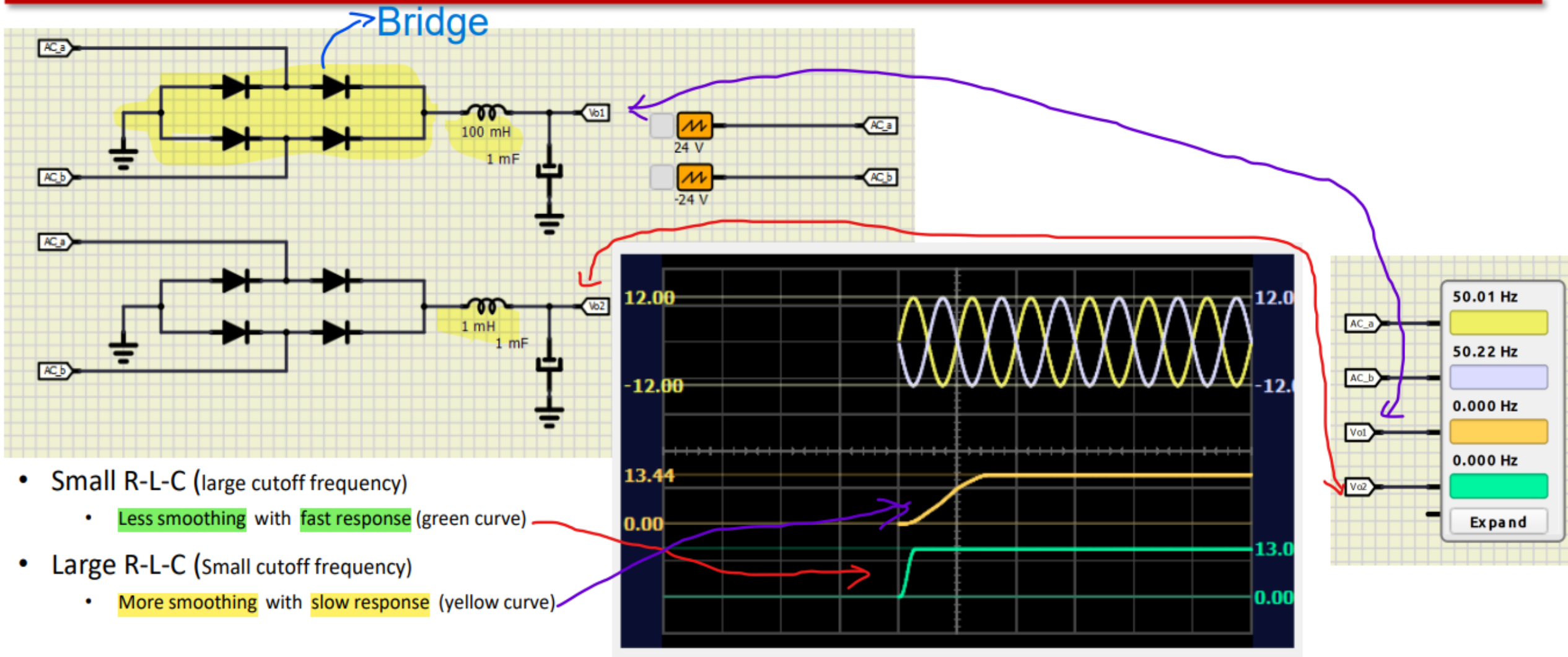



# Effect of load change

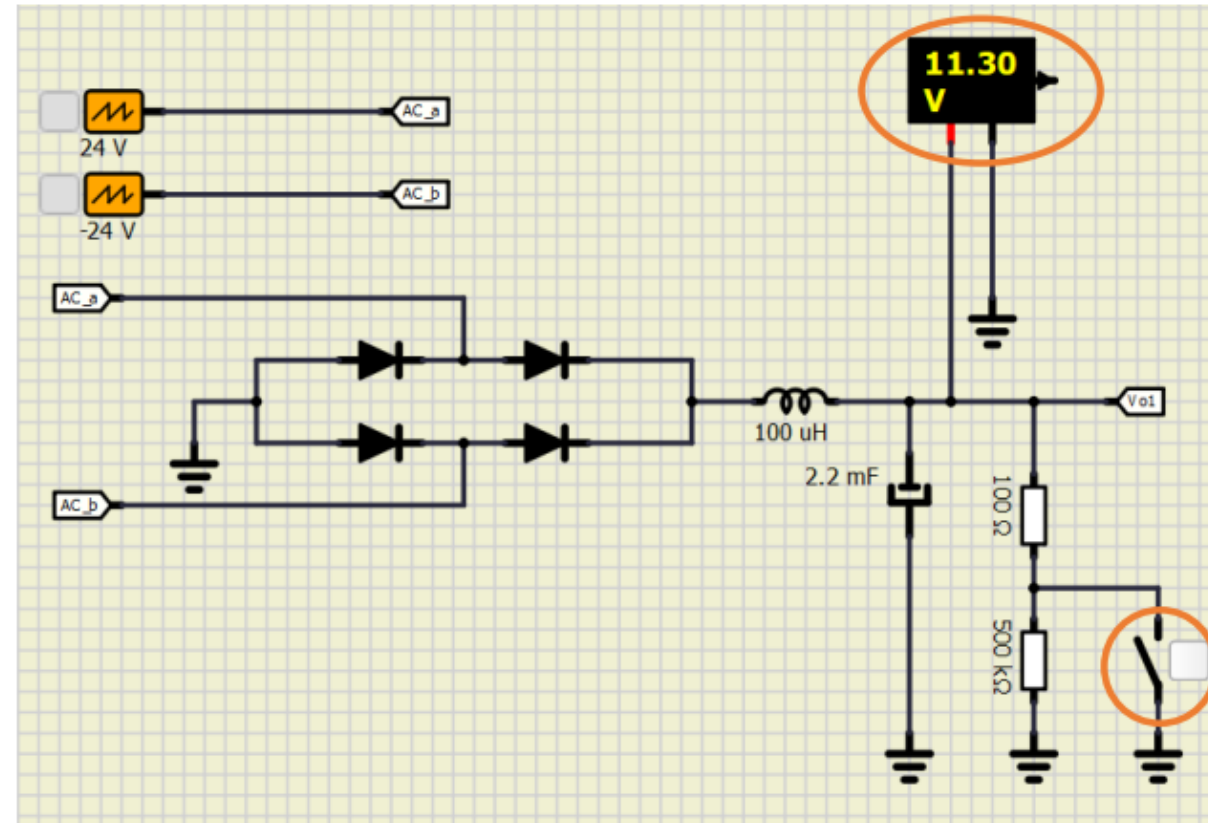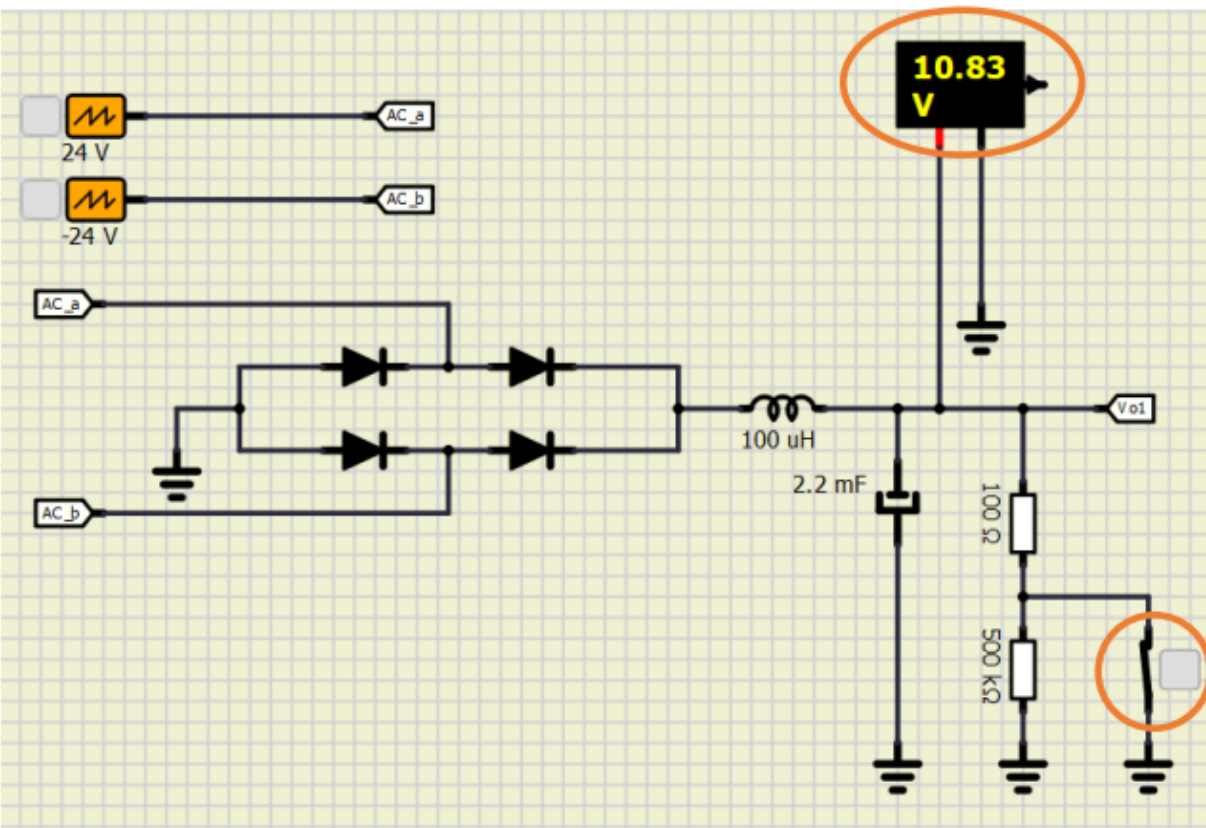

- A change on the output voltage with load change

# Linear regulator

To solve the problem of loading effect

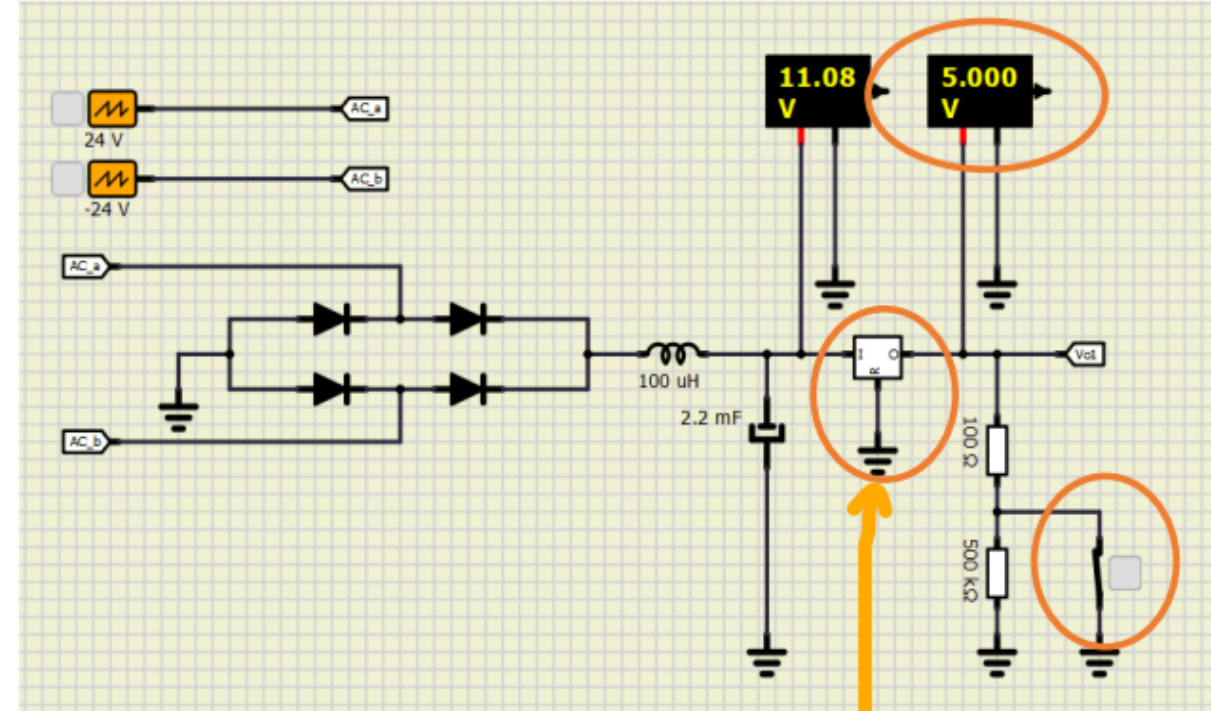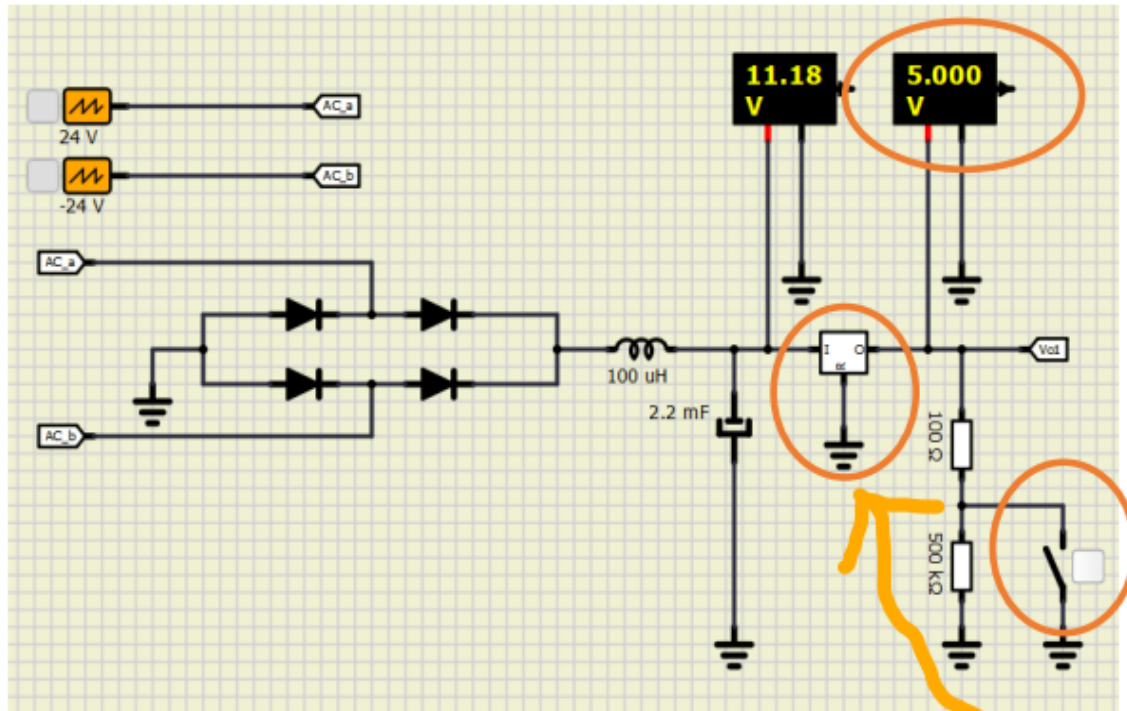

**7805 VOLTAGE REGULATOR**

but it has a disadvantage  
that it becomes very hot , so it has small efficiency





# Switched-mode power supply

it has high Efficiency

A switched-mode power (SMPS) is an electronic power supply that incorporates a switching regulator to convert electrical power efficiently.


this DC value is a function of the Duty Cycle  
if we change it we change the DC Output  
that give us a great flexibility

1- Rectifying input signal

2 - enter it to High Frequency switch to cut it and convert it to AC again

3- step down it by a power transformer

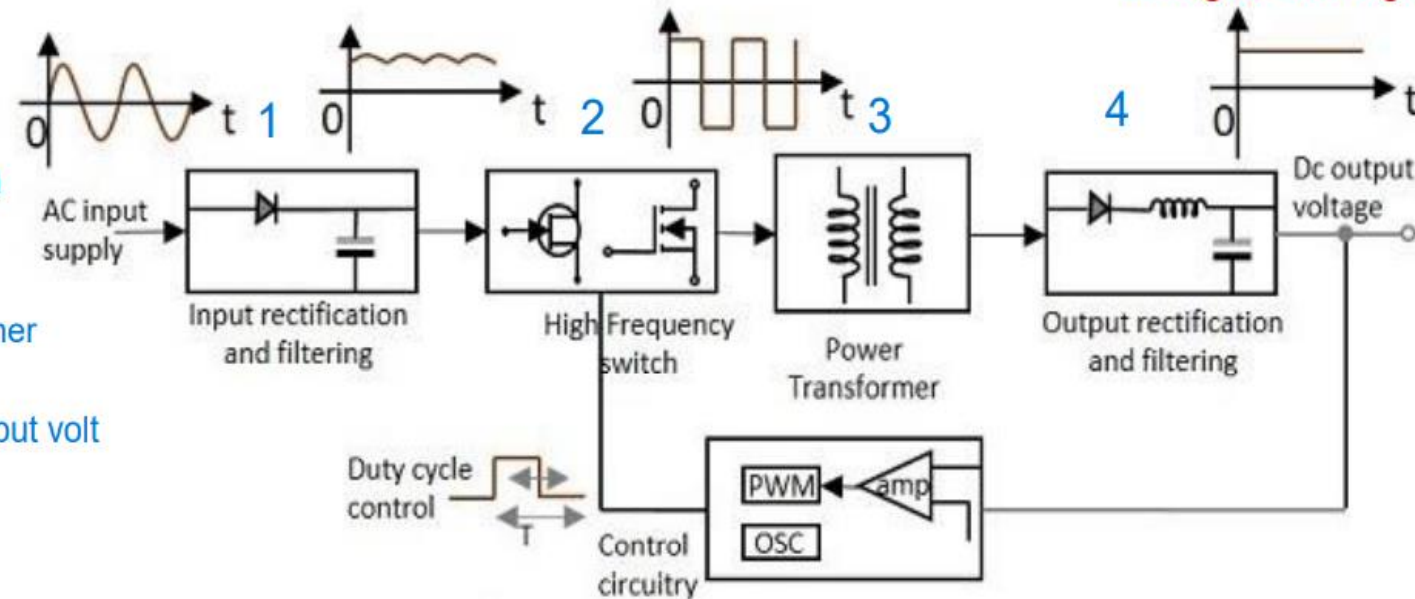4 - Rectifying it again to get DC output volt




Functional block diagram of SMPS


# Switched-mode power supply
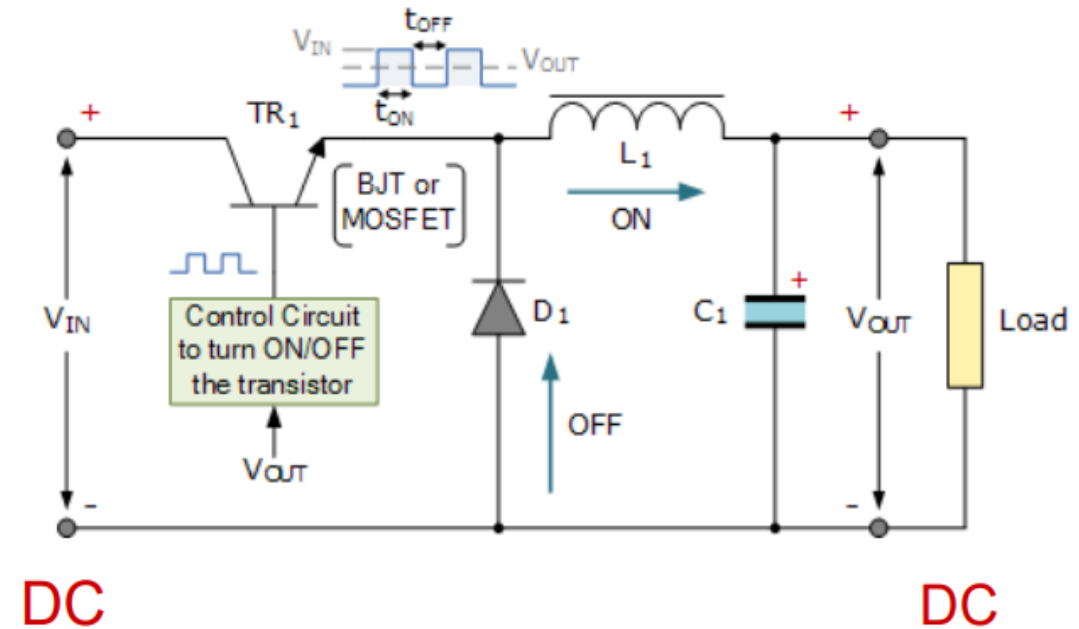
## Buck converter

The Buck switching regulator is a type of switch mode power supply circuit that is designed to efficiently **reduce DC voltage** from a **higher voltage** to a **lower one**, that is it subtracts or “Bucks” the supply voltage, thereby **reducing the voltage** available at the output terminals **without changing the polarity**. In other words, the buck switching regulator is a **step-down** regulator circuit, so for example a buck converter can convert say, +12 volts to +5 volts.


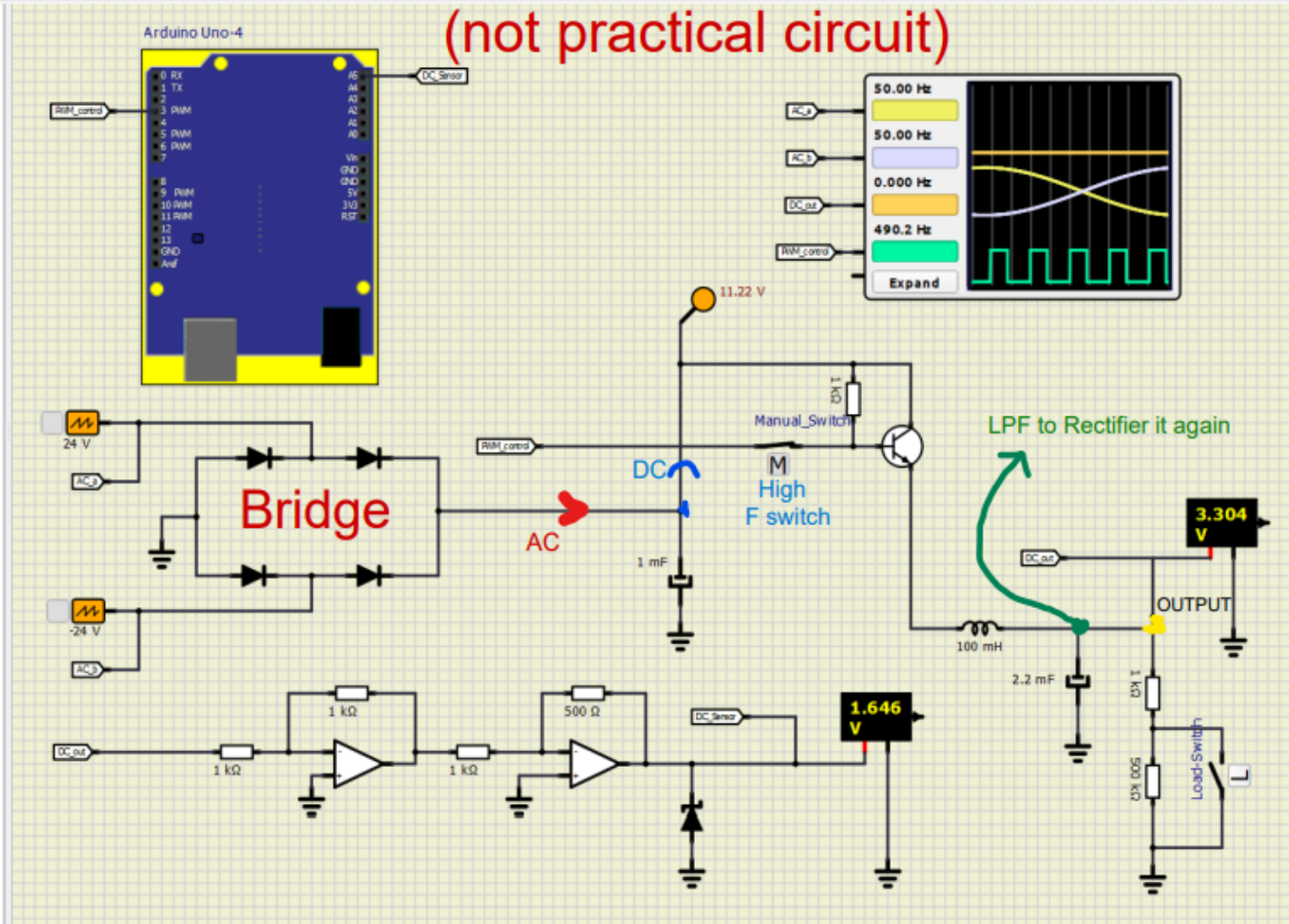
# Switched-mode power supply using Arduino (Concept Ct.) (Target 3.3 Volt)







(cont.)

```

25 //float Kp=0.005; float Ki=0.01; float Kd=0 ; // Slow
26 float Kp=0.01; float Ki=0.1; float Kd=0 ; // Fast
27
28 void loop(void) {
29     float v=read_val();
30     e=r-v;
31     up=Kp*e;
32     ui=ui+Ki*e;
33     ud=Kd*(e-e_old);
34     u=up+ui+ud;
35     if ( (u>MAX_U) || (u<MIN_U) ) {
36         ui=ui_old;
37         u=up+ui+ud;
38     }
39     e_old=e;
40     ui_old=ui;
41     Serial.print("r= ");    Serial.print(r);
42     Serial.print(", v= ");  Serial.print(v);
43     Serial.print(", u= ");  Serial.print(u);
44     Serial.print(", e= ");  Serial.println(e);
45     set_val(u);
46 }

```

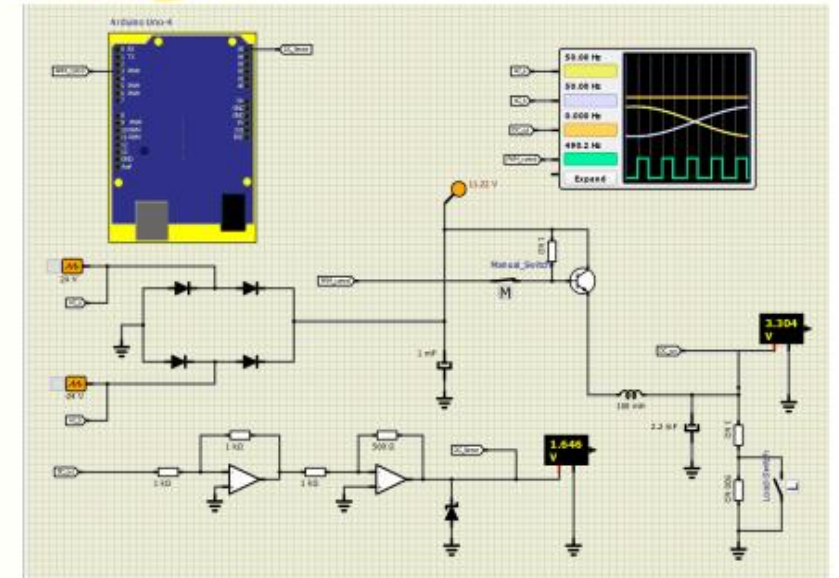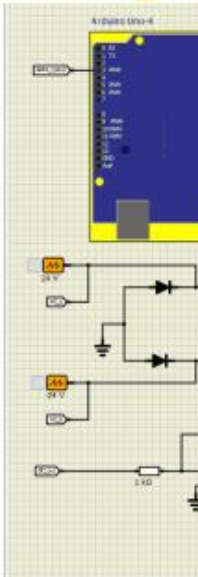

pwm compensates load effect  
to adjust volt at 3.3 v

	Linear Regulator	Switch Mode Power Supply
Advantages	<p><b>Simple application:</b> can be implemented as an entire package and added to a circuit with only two additional filter capacitors.</p> <p><b>Low cost:</b> If your device requires a power output of less than 10W.</p> <p><b>Low noise/ripple:</b> have a very low output voltage ripple and high bandwidth. This makes them ideal for any noise-sensitive applications including communication and radio devices.</p>	<p><b>Small form factor:</b> it operates at a high frequency reduces its volume and weight ,This allows a switching power supply to enjoy a much smaller form factor than linear regulators</p> <p><b>High efficiency:</b> it's made without dissipating excessive amounts of heat. efficiency can be as high as 85%-90%</p> <p><b>Flexible applications:</b> Additional windings can be added to a switching power supply to provide more than one output voltage.</p>
Disadvantages	<p><b>Limited flexibility:</b> can only be used to step down voltage, For an AC-DC power supply, a transformer with rectification and filtering will need to be placed before the linear power supply which will add to overall costs and effort.</p> <p><b>Limited outputs:</b> Linear regulated power supplies only provide one output voltage.</p> <p><b>Poor efficiency:</b> The average linear regulated device achieves an efficiency between 30%-60% due to heat dissipation.</p>	<p><b>Complicated design.</b> Compared to linear regulators, planning and designing a switching power supply is typically reserved for power specialists.</p> <p><b>High-frequency noise:</b> The switching operation of the MOSFET within a switching power supply provides high-frequency noise in the output voltage. This often requires the use of RF shielding and EMI filters in noise-sensitive devices.</p> <p><b>Higher cost:</b> For lower power outputs of 10W or less, it's cheaper to use a linear regulated power supply.</p>

# AC Dimmer




2- produce it as pulses of (0,1) forward it to arduino to know start and end of phase

1- take AC signal rectifier it

3 - then arduino will produce PWM pulse based on start and end of phase to switch on and off

**Auto AC Dimmer**


You Can use Bridge Rectifier IC DB107

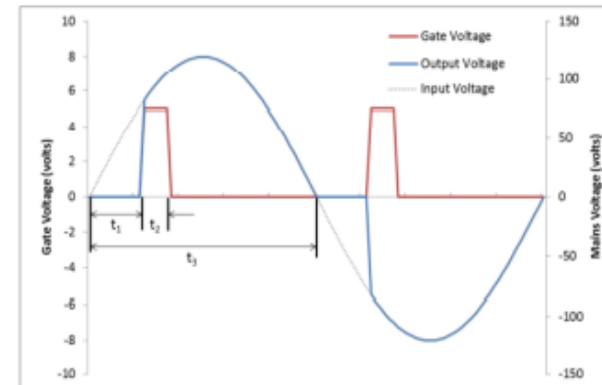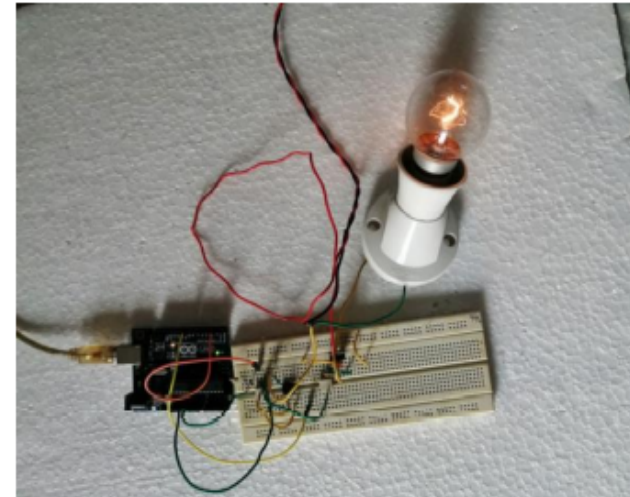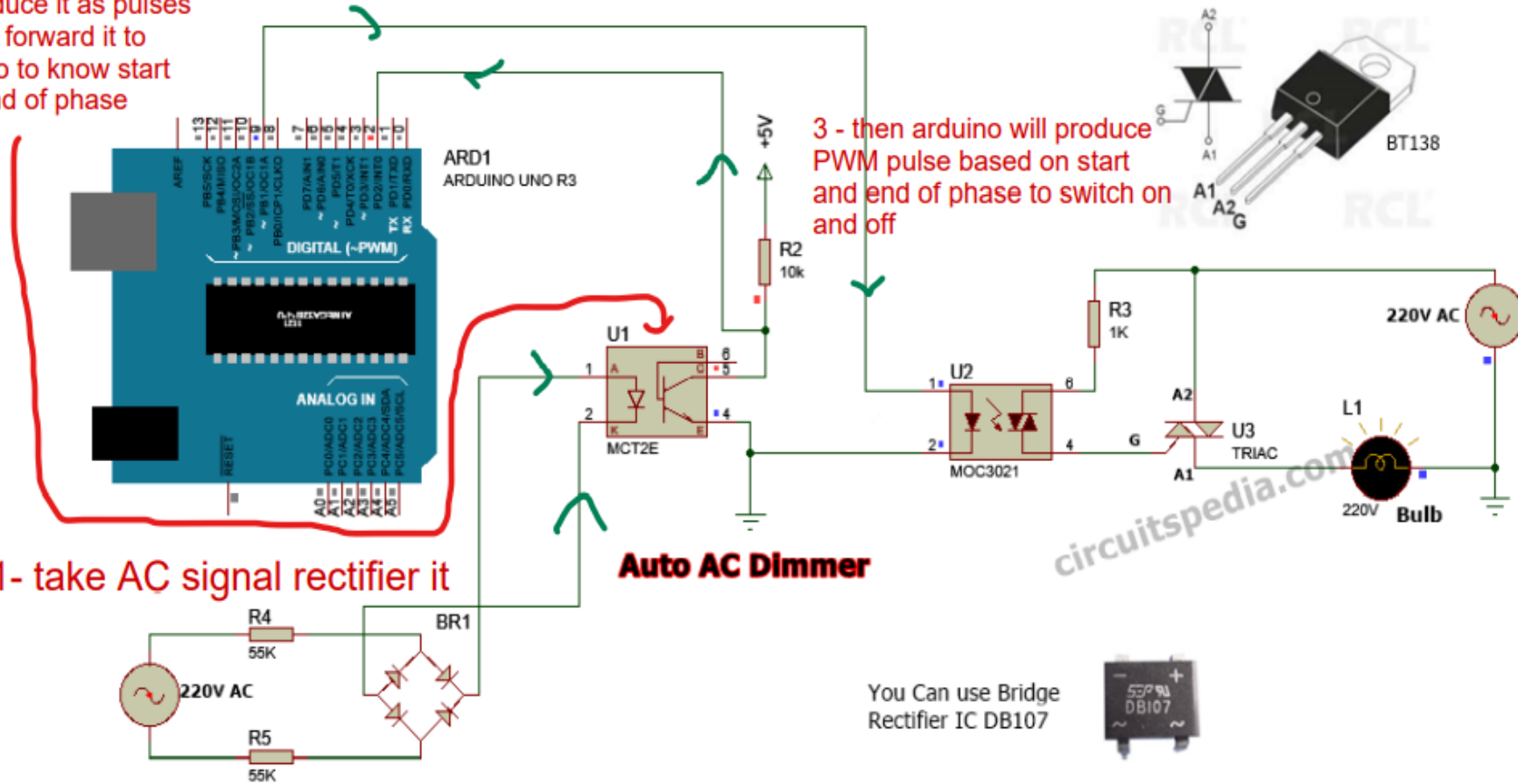





# Variable-frequency drive VFD

(AC Inverter)

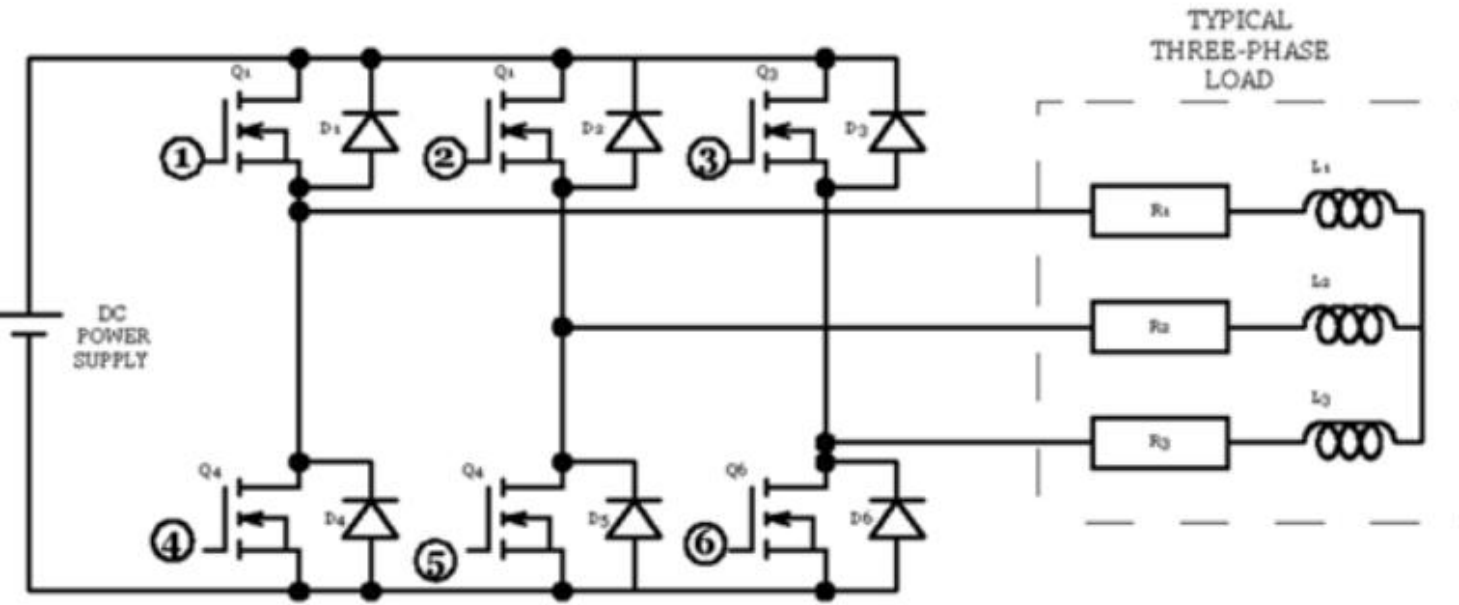


Convert from DC to 3 phase AC

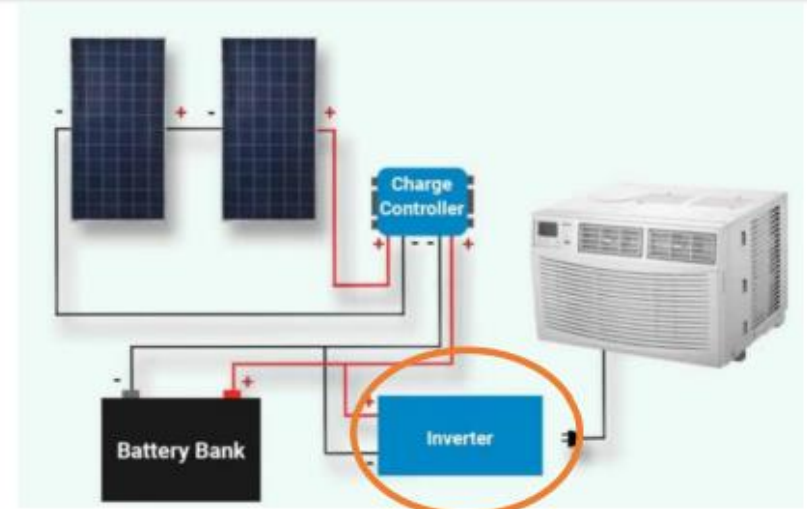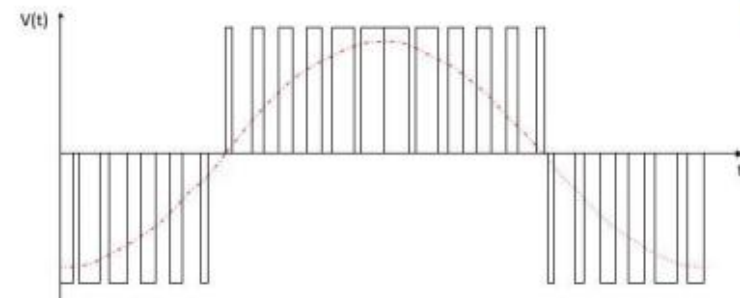

# Variable-frequency drive VFD

## (AC Inverter) (Cont.)

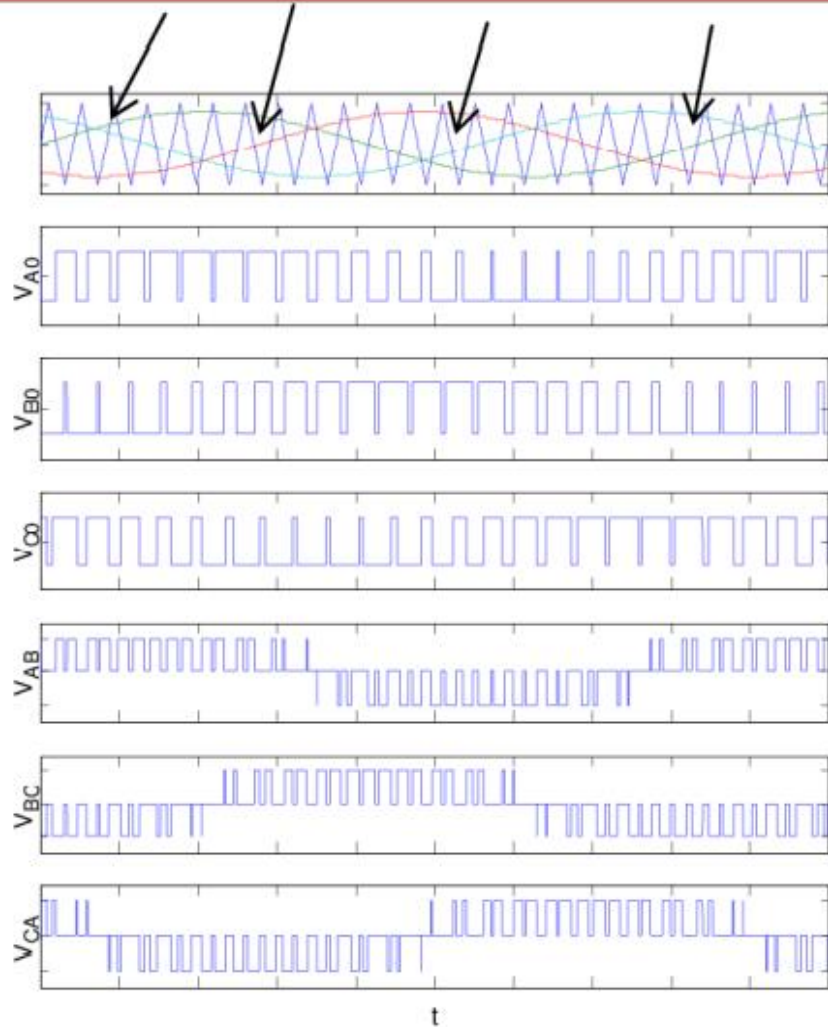

PWM signals  
out of phases as we like

